



Low Noise 0.6% Accuracy 200mA LDO

The RP100x Series are CMOS-based LDO regulators featuring 200mA output. RP100x features supply current as low as 18μA, which is far lower than existing lines. Due to a built-in 0.87Ω (at Vsετ=2.8V) on-resistor, RP100x can provide a low dropout voltage. RP100x also features an excellent line transient response, ripple rejection at 75dB, and low noise. The output voltage accuracy is as high as \pm 0.6% and the temperature drift coefficient of output voltage is low at \pm 30ppm/°C.

FEATURES


- Supply Current (Iss) ------Typ. 18μA (VIN=VSET+1.0V)
- Standby Current (Istandby)Typ. 0.1μA (Same as above, CE="L")
- ◆ Dropout Voltage (VDIF)Typ. 0.13V (IOUT=150mA, VSET=2.8V)
- Ripple Rejection (RR).....Typ. 75dB (f=1kHz)
- Input Voltage Range (V_{IN})------1.7V to 5.25V
- Output Voltage Range (Vout) 1.2V to 3.3V (Internally fixed)

- Output Voltage Accuracy-----± 0.6%
- Temp. coeff. of Output Voltage Typ. ± 30ppm/°C
- Line RegulationTyp. 0.02%/V
- Fold-back Protection Circuit Current limit Typ. 40mA
- Auto-discharge Function D Version
- PackagesDFN(PLP)1612-4, SOT-23-5
- Ceramic capacitors can be used. ... 1 µF or more

BLOCK DIAGRAMS


RP100xxx1B

(Without Auto-discharge function)

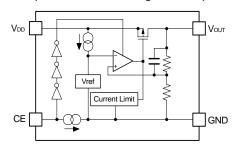

RP100xxx1D

(With Auto-discharge function)

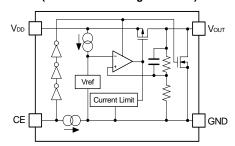

SELECTION GUIDES

Halogen Free	Package	Q'ty per Reel	Part No.
H/F	DFN(PLP)1612-4	5,000 pcs	RP100Kxx1*-TR
H/F	SOT-23-5	3,000 pcs	RP100Nxx1*-TR-FE

- xx : Specify the output voltage within the range of 1.2V (12) to 3.3V (33) in 0.1V steps.
- : Select from (B) without auto-discharge function or (D) with auto-discharge function.

PACKAGES (Top View)

DFN(PLP)1612-4	SOT-23-5		
1 2	5 4 1 2 3		
1	1 VDD		


1	Vouт
2	GND
3	CE
4	V _{DD}

^{*)} The tab is substrate level (GND).



TYPICAL CHARACTERISTIC

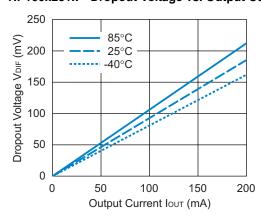RP100x281x Dropout Voltage vs. Output Current



APPLICATIONS

- Power source for hand-held communication equipment, cameras, and VCRs
 Power source for battery-powered equipment
- Power source for home appliances

No FK-140-121001 CMOS LDO Regulator



1. The products and the product specifications described in this document are subject to charge discontinuation of production without notice for reasons such as improvement. Therefore, before deciding to use the products, please refer to Ricoh sales representatives for the latest information thereon.

Mall.com

- 2. The materials in this document may not be copied or otherwise reproduced in whole or in part without prior written consent of Ricoh.
- 3. Please be sure to take any necessary formalities under relevant laws or regulations before exporting or otherwise taking out of your country the products or the technical information described herein.
- 4. The technical information described in this document shows typical characteristics of and example application circuits for the products. The release of such information is not to be construed as a warranty of or a grant of license under Ricoh's or any third party's intellectual property rights or any other rights.
- 5. The products listed in this document are intended and designed for use as general electronic components in standard applications (office equipment, telecommunication equipment, measuring instruments, consumer electronic products, amusement equipment etc.). Those customers intending to use a product in an application requiring extreme quality and reliability, for example, in a highly specific application where the failure or misoperation of the product could result in human injury or death (aircraft, spacevehicle, nuclear reactor control system, traffic control system, automotive and transportation equipment, combustion equipment, safety devices, life support system etc.) should first contact us.
- 6. We are making our continuous effort to improve the quality and reliability of our products, but semiconductor products are likely to fail with certain probability. In order to prevent any injury to persons or damages to property resulting from such failure, customers should be careful enough to incorporate safety measures in their design, such as redundancy feature, firecontainment feature and fail-safe feature. We do not assume any liability or responsibility for any loss or damage arising from misuse or inappropriate use of the products.
- 7. Anti-radiation design is not implemented in the products described in this document.
- Please contact Ricoh sales representatives should you have any questions or comments concerning the products or the technical information.



For the conservation of the global environment, Ricoh is advancing the decrease of the negative environmental impact material. After Apr. 1, 2006, we will ship out the lead free products only. Thus, all products that will be shipped from now on comply with RoHS Directive. Basically after Apr. 1, 2012, we will ship out the Power Management ICs of the Halogen Free products only. (Ricoh Halogen Free products are also Antimony Free.)

RICOH

RICOH COMPANY, LTD. **Electronic Devices Company**

http://www.ricoh.com/LSI/

RICOH COMPANY, LTD.

Electronic Devices Company

Higashi-Shinagawa Office (International Sales)
3-32-3, Higashi-Shinagawa, Shinagawa-ku, Tokyo 140-8655, Japan
Phone: +81-3-5479-2857 Fax: +81-3-5479-0502

RICOH EUROPE (NETHERLANDS) B.V.

Semiconductor Support Centre

"Nieuw Kronenburg" Prof. W.H. Keesomlaan 1, 1183 DJ, Amstelveen, The Netherlands P.O.Box 114, 1180 AC Amstelveen Phone: +31-20-5474-309 Fax: +31-20-5474-791

RICOH ELECTRONIC DEVICES KOREA Co., Ltd.

11 floor, Haesung 1 building, 942, Daechidong, Gangnamgu, Seoul, Korea Phone: +82-2-2135-5700 Fax: +82-2-2135-5705

RICOH ELECTRONIC DEVICES SHANGHAI Co., Ltd.

Room403, No.2 Building, 690#Bi Bo Road, Pu Dong New district, Shanghai 201203, People's Republic of China Phone: +86-21-5027-3200 Fax: +86-21-5027-3299

RICOH COMPANY, LTD.

Electronic Devices Company

● Taipei office
Room109, 10F-1, No.51, Hengyang Rd., Taipei City, Taiwan (R.O.C.)
Phone: +886-2-2313-1621/1622 Fax: +886-2-2313-1623